MAME - MONU ENTRY NO - 2020CS50432

Subtabk-7


Jask is to design a multiplier circuit and embed It with multicycle design.

Multicycle design with multiplier.

Multiplier: Unit which furforms all multiplication operations on values and outputs appropriate answer to out 1 and out 2 port.

Deta Cincuits. logics to connect all the

Further details are below:

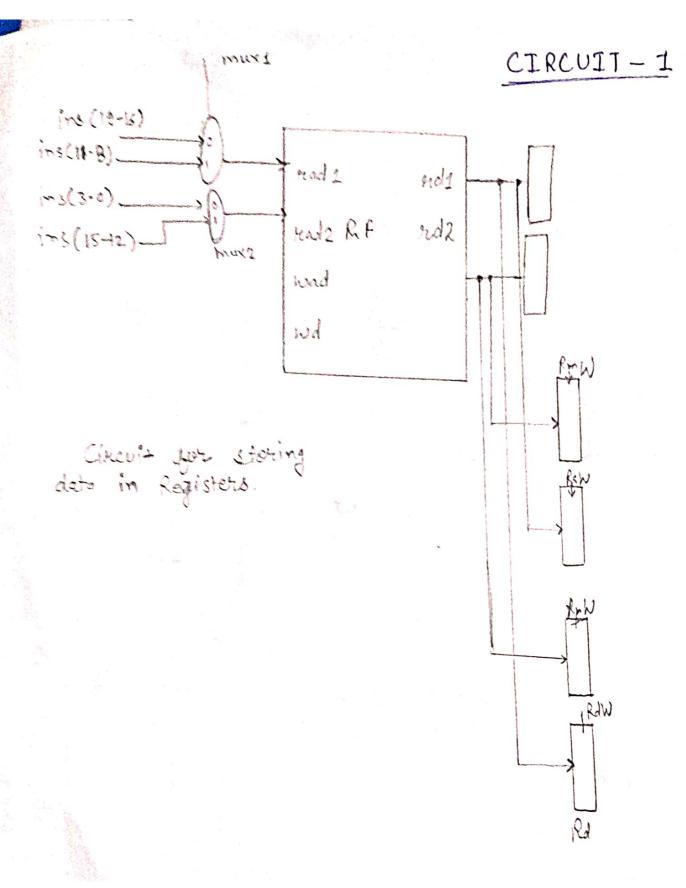

Circit-2: for reading data from registers and then applying operations on data to get apropriate solutions seconding to instruction.

signal